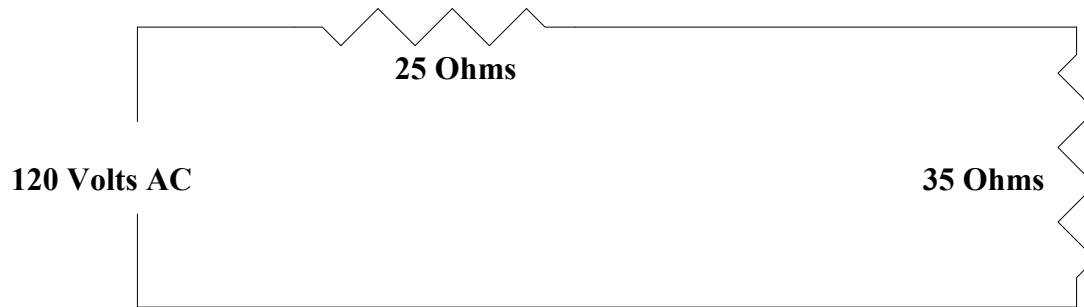




NAME: _____ DATE: _____
(Please Print)

RESISTOR NETWORK AND OHMS LAW PRACTICE EXAM
(See formulas at the back of this exam)



1. Based on the drawing above, what is the total circuit resistance?

Answer _____

2. Based on the drawing above, what is the current flow in the circuit?

Answer _____

3. Based on the drawing above, what is the voltage drop across the 25 ohm resistor?

Answer _____



4. Based on the drawing above, what is the total circuit resistance?

Answer _____

5. Based on the drawing above, what is the total current flow in the circuit?


Answer _____

6. Based on the drawing above, what is the current flow through the 6 ohm resistor?

Answer _____

7. Based on the drawing above, how much power is consumed by the 12 ohm resistor?

Answer _____

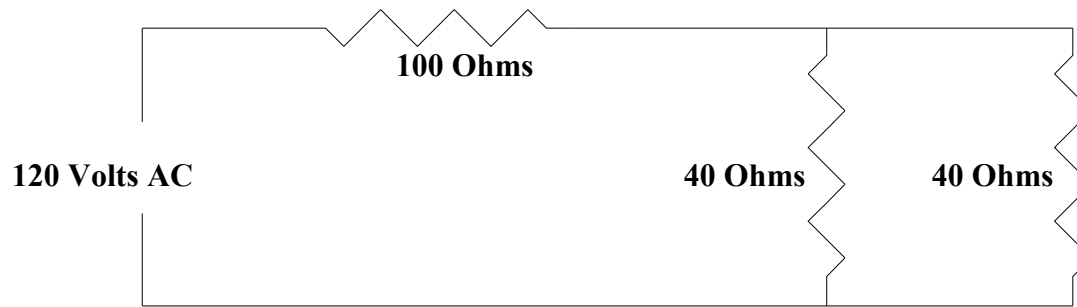

8. Based on the drawing above, what is the total circuit resistance?


Answer _____

9. Based on the drawing above, what is the total current flow in the circuit?

Answer _____

10. Based on the drawing above, what is the voltage across one of the 40 ohm resistors?

Answer _____

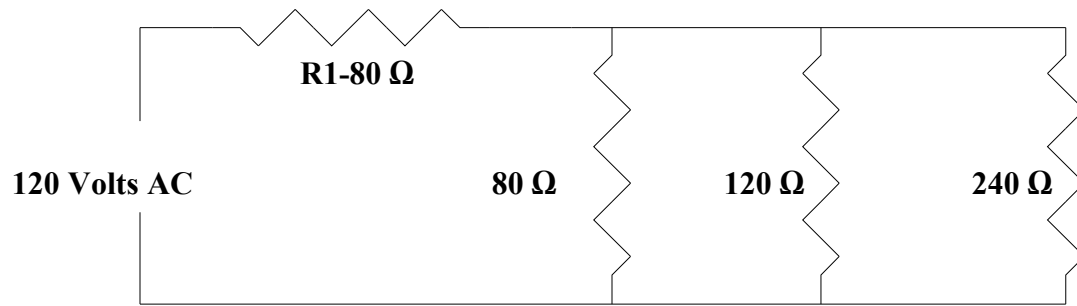


11. Based on the above drawing, how much current is flowing through the 120 ohm resistor?

Answer _____

12. Based on the above drawing, what is the voltage drop across R1?


Answer _____

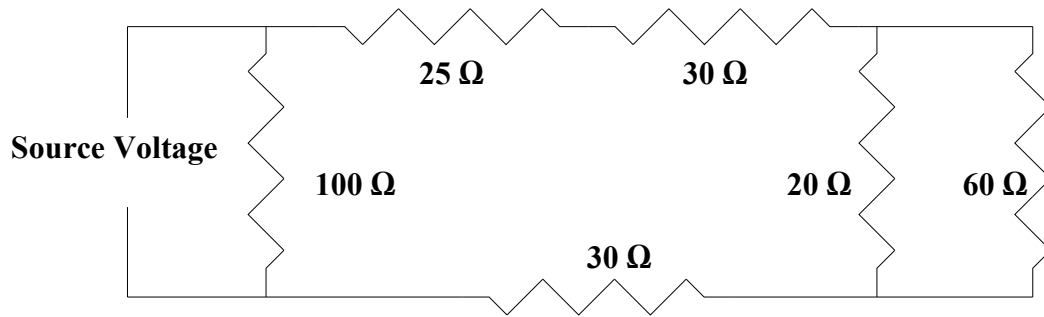


13. Based on the drawing above, what is the equivalent circuit resistance?

Answer _____

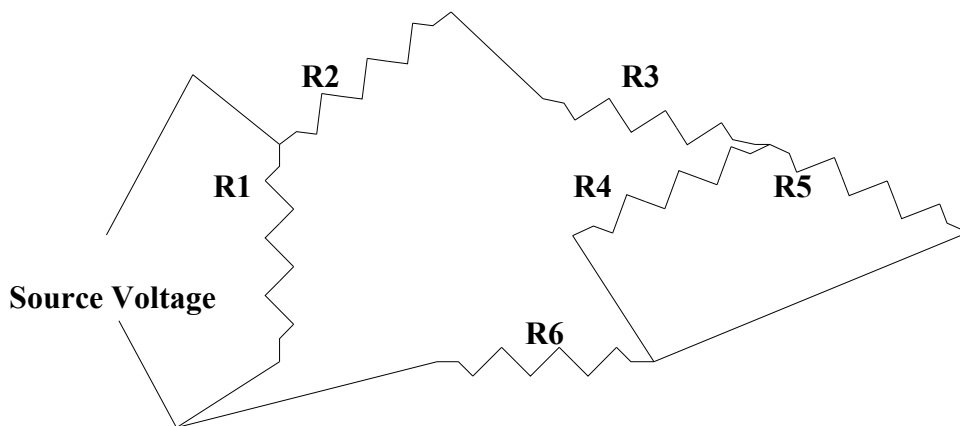14. Take a look at the resistor network below. What do you notice about this diagram?



Answer _____

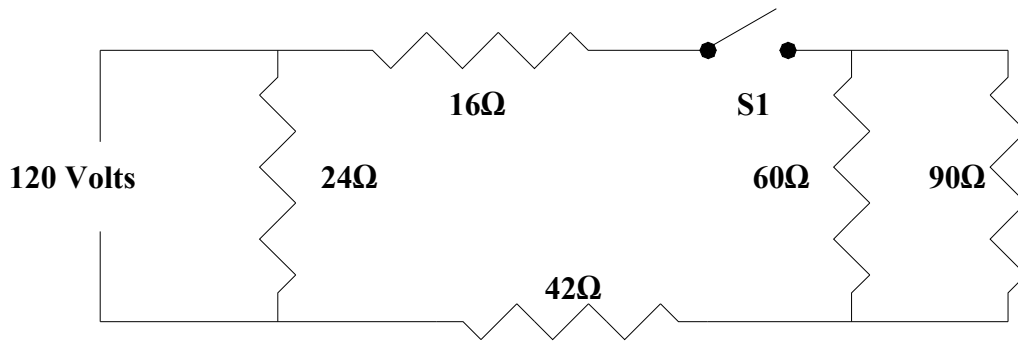


15. Based on the drawing above, what is the equivalent circuit resistance if S1 is closed?

Answer _____

16. Based on the drawing above, what is current flow through the circuit if S1 is open?

Answer _____

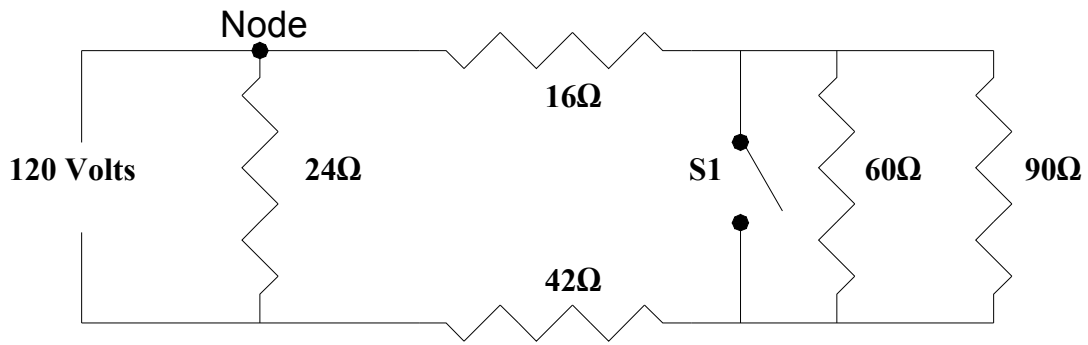

17. Based on the drawing above, what is the equivalent circuit resistance if S1 is closed?

Answer _____

18. Based on the drawing above, what is the current flow through the 16 ohm resistor if S1 is open?

Answer _____

Electrical Exam Formulas

1) $P = I \times E$, $P(3 \text{ Phase}) = I \times E \times 1.73$

2) $E = I \times R$

3) $P = I \times E \times (\text{Pf})$

4) $V_d = (2 \times K \times D \times I) / \text{CM}$

5) $V_d (3 \text{ Phase}) = (1.73 \times K \times D \times I) / \text{CM}$

6) Parallel Resistors

$$R_t = \frac{1}{1/R_1 + 1/R_2 + \dots + 1/R_n}$$

OR

$$R_t = \frac{R_1 \times R_2}{R_1 + R_2}$$

7) Series Resistors

$$R_t = R_1 + R_2 + \dots + R_n$$

P= Power in watts

I=Current in amps

E=Voltage in volts

R=Resistance in ohms, R_t =Total resistance

V_d =Voltage drop in volts

Pf=Power factor

D=Distance (one way) in feet

CM=Circular mils of wire (Ch. 9, Table 8)

K=Resistance of a circular mil-foot (Approx. 12.9 for Cu, 21.2 for Al)

HP=746 Watts

